


Session 2: The loop unrolling architecture

Antonio de la Piedra

Institute for Computing and Information Sciences – Digital Security
Radboud University Nijmegen

February 25, 2015

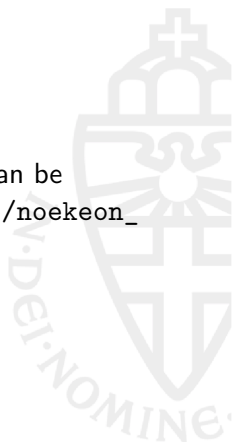- Introduce the loop unrolling architecture
- We rely on NOEKEON
- The implementation that is used in this session can be download from https://github.com/adelapie/noekeon_loop/archive/master.zip



- ① Area
- ② The loop unrolling architecture
- ③ A loop unrolling architecture for NOEKEON
 - $K = 2$
 - $K = 4$
- ④ Area/Throughput ratio



How this is related to your projects

- 1 You can see this architecture between the iterative and the pipeline one in terms of area and throughput.
- 2 Once you have implemented an iterative architecture of the block cipher you have chosen, feel free to implement a loop unrolling one, analyze the speed up in throughput.

- There is a new tutorial about creating and testing combinational circuits at <https://rucryptoengineering.files.wordpress.com/2015/02/tutorial2.pdf>
 - Follow it before start implementing the functions of the round of the block cipher you have chosen.
 - It considers you have succeeded with the first one.
- The theory behind this chapter is based on
 - *Cryptographic Engineering, Koc, Cetin Kaya (Ed.) 2009*

Part I: Design parameters



Area is related to:

- Cost: typically proportional to the circuit area.
- Maximum area limit: related to cost, fabrication technology, power consumption.




Units:

- Application-Specific Integrated Circuit (ASIC): μm^2 , transistor count, logic gate count
- Field-Programmable Gate Array (FPGA): number of configurable logic blocks (CLB), also related to embedded blocks utilization e.g. BRAM, DSPs, etc.
 - **More with Pedro later.**

Part II: The loop unrolling architecture



- The combinational part of the circuit implements K rounds of the cipher.
- The number of cycles required for encrypting data block is decreased by a factor K .

 

 


Figure : Loop unrolling for $K = 2$

- The number of required clock cycles is reduced by a K factor.

Throughput

$$\text{Throughput} = \frac{\text{blocksize}}{\frac{\text{rounds}}{K} \cdot T_{CLK}}$$

- The minimum clock period increases by a factor smaller by K but throughput is increased, latency decreased.

Latency

$$\text{Latency} = \frac{\text{rounds}}{K} \cdot T_{CLK}$$


Disadvantages:

- The area increases proportional to the number of unrolled rounds.
- The number of subkeys k_i that are used by cycle must be stored, which increases the area according to the factor K . For instance, in the case of AES-128 (ten rounds, 128 bit keys):
 - For $K = 2$, 5 cycles, 256 bits
 - For $K = 5$, 2 cycles, 640 bits


Part III: A loop unrolling architecture for NOEKEON



 - Replicate the round by a factor of K
- Adapt key schedule and round constant generation according to K




 - We rely on direct mode: no key schedule
 - We don't need to store the subkeys in this case
- We need to generate more than one round constant:
 - $K = 2$
 - $K = 4$




Round constants $K = 2$

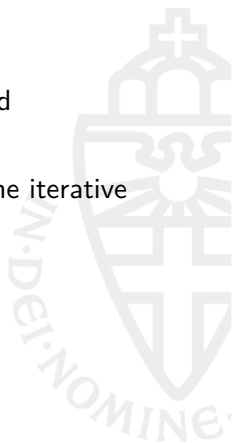- In each cycle, two rounds of the cipher are applied
- We need two constants per cycle
- The round constant generator that was used in the iterative design cannot be used




Round constants $K = 2$

 - Create two shift registers
- Initialize them with the correspondent round constants



 - e.g. for encryption:
 - $[80, 1b, 36, 6c, d8, ab, 4d, 9a, 2f, 5e, bc, 63, c6, 97, 35, 6a]$
- With two shift registers:
 - $RC_0 = [80, 36, d8, 4d, 2f, bc, c6, 35]$
 - $RC_1 = [1b, 6c, ab, 9a, 5e, 63, 97, 6a]$



Round constants $K = 4$

- e.g. for encryption:
 - $[80, 1b, 36, 6c, d8, ab, 4d, 9a, 2f, 5e, bc, 63, c6, 97, 35, 6a]$
- With four shift registers:
 - $RC_0 = [80, d8, 2f, c6]$
 - $RC_1 = [1b, ab, 5e, 97]$
 - $RC_2 = [36, 4d, bc, 35]$
 - $RC_3 = [6c, 9a, 63, 6a]$



Shift register for round constants

```
entity rc_shr is
    port(clk : in std_logic;
          rst : in std_logic;
          rc_in : in std_logic_vector(63 downto 0);
          rc_out : out std_logic_vector(7 downto 0));
end rc_shr;

architecture Behavioral of rc_shr is
    signal sh_reg : std_logic_vector(63 downto 0);
begin
    pr_shr: process(clk, rst)
    begin
        if rising_edge(clk) then
            if rst = '1' then
                sh_reg <= rc_in;
            else
                sh_reg <= sh_reg(55 downto 0) & sh_reg(63 downto 56);
            end if;
        end if;
    end process;

    rc_out <= sh_reg(63 downto 56);
end Behavioral;
```

Shift register for round constants

```
begin
    signal init_val_shr_0 : std_logic_vector(63 downto 0);
    signal init_val_shr_1 : std_logic_vector(63 downto 0);

    init_val_shr_0 <= X"8036d84d2fbcc635";
    init_val_shr_1 <= X"1b6cab9a5e63976a";

    RC_SHR_0 : rc_shr port map (clk, rst, init_val_shr_0, rc_s);
    RC_SHR_1 : rc_shr port map (clk, rst, init_val_shr_1, rc_2_s);

    rc_ext_s <= X"000000" & rc_s;
    rc_2_ext_s <= X"000000" & rc_2_s;
```

Rounds for $K = 2$

```
signal stage_0_a_0_out_s : std_logic_vector(31 downto 0);  
signal stage_0_a_1_out_s : std_logic_vector(31 downto 0);  
signal stage_0_a_2_out_s : std_logic_vector(31 downto 0);  
signal stage_0_a_3_out_s : std_logic_vector(31 downto 0);
```

Rounds for $K = 2$

```
ROUND_F_0 : round_f port map (enc,  
                                rc_ext_s ,  
                                a_0_in_s ,  
                                a_1_in_s ,  
                                a_2_in_s ,  
                                a_3_in_s ,  
                                k_0_mux_s ,  
                                k_1_mux_s ,  
                                k_2_mux_s ,  
                                k_3_mux_s ,  
                                stage_0_a_0_out_s ,  
                                stage_0_a_1_out_s ,  
                                stage_0_a_2_out_s ,  
                                stage_0_a_3_out_s);  
  
ROUND_F_1 : round_f port map (enc,  
                                rc_2_ext_s ,  
                                stage_0_a_0_out_s ,  
                                stage_0_a_1_out_s ,  
                                stage_0_a_2_out_s ,  
                                stage_0_a_3_out_s ,  
                                k_0_mux_s ,  
                                k_1_mux_s ,  
                                k_2_mux_s ,  
                                k_3_mux_s ,  
                                a_0_out_s ,  
                                a_1_out_s ,  
                                a_2_out_s ,  
                                a_3_out_s);
```


- Four shift registers
- Four rounds interconnected
- *noekeon_loop_k_4.vhd*



Part IV: Area and throughput analysis



Number of cycles per round

- For $K = 2$, $16/2 = 8$ cycles
- For $K = 4$, $16/4 = 4$ cycles



- Iterative (Session 1):
 - Area: 264 FFs, 966 LUTs, $N = 16$
 - Max. Freq: 144.211 MHz
- Loop unrolling $K = 2$:
 - Area: 355 FFs, 1,496 LUTs, $N = 8$
 - Max. Freq: 97.404 MHz
- Loop unrolling $K = 4$:
 - Area: 367 FFs, 2,829 LUTs, $N = 4$
 - Max. Freq: 56.461 MHz



Throughput iterative

$$\text{Throughput} = \frac{\text{blocksize}}{\text{rounds} \cdot T_{\text{CLK}}}$$

Throughput loop unrolling

$$\text{Throughput} = \frac{\text{blocksize}}{\frac{\text{rounds}}{K} \cdot T_{\text{CLK}}}$$

- Iterative (Session 1)
 - $\frac{128}{16 \cdot \frac{1}{144.211 \cdot 10^6}} = 1.153,7 \text{ Gbits/s}$
- Loop unrolling $K = 2$
 - $\frac{128}{\frac{16}{2} \cdot \frac{1}{97.404 \cdot 10^6}} = 1.558,5 \text{ Gbits/s}$
- Loop unrolling $K = 4$:
 - $\frac{128}{\frac{16}{4} \cdot \frac{1}{56.461 \cdot 10^6}} = 1.806,8 \text{ Gbits/s}$



- Rely on the iterative architecture when the area is the only parameter you care about.
- Rely on pipelining when you only care about throughput (next week).
- Consider the loop unrolling architecture as an intermediate step between both.
 - You should start with a full unrolled architecture for pipelining.

Questions?

